

## University of British Columbia Electrical and Computer Engineering Electrical and Biomedical Engineering Design Studio ELEC291/ELEC292

## Adding WAV Sound to the ATMega328P

Copyright © 2021, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

The diagram below shows the connections required to add WAV sound to the ATMega328P using PWM. Please note that the power pin of the ATMega328P is connected to 3.3V.



