

#### University of British Columbia Electrical and Computer Engineering ELEC291/ELEC292

# Lab 6: New Microcontroller Setup.

Dr. Jesús Calviño-Fraga P.Eng.
Department of Electrical and Computer Engineering, UBC
Office: KAIS 3024

E-mail: jesusc@ece.ubc.ca Phone: (604)-827-5387

March 10, 2023

Lab #6

Copyright @ 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

1

#### Requirements & Comments

- Lab #6 requirements are the same as Lab #4 (for ELEC291 students) but microcontroller system must not be 8051!
- Programmed in C.
- · Work with a partner.
- Good start for Project #2

## Getting the Parts for Lab #6 and Project #2

- Buy the kit (one per team, CAD 80\$) by visiting:
  - <u>https://eng-services.ece.ubc.ca/course-support/2022-winter-term-2/elec291/</u>
  - Password: ee291-3 2023
- Bring proof of payment to EECE stores (MCLD 1032) to pick up you kit.

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, revised without explicit written permission from the convigant owner.

3

## Getting Started with a New Microcontroller System

- 1. Obtain/assemble the hardware. Also documentation: datasheets & manuals.
- 2. Obtain/install the development environment. Also documentation like manuals.
- 3. Obtain/install a means of putting the 'firmware' in the hardware ("Flash Load"). May require additional hardware tools and software.
- 4. Settle a workflow. Also: examples, application notes, and forums.

4

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, o revised without explicit written permission from the copyright owner.

## Getting Started with a New Microcontroller System

- In this course is not too difficult. Instructions provided for:
  - PIC32MX130: DIP-28. 64k flash. Microchip. MIPS architecture.
  - MSP430G2553: DIP-20. 16k flash. Texas Instruments.
     MSP430 architecture.
  - ATMEGA328P: DIP-28. 32k flash. Formerly Atmel, now Microchip. AVR architecture.
  - STM32L051: LQFP32. 64k flash. ST Microelectronics.
     ARM architecture.
  - LPC824: TSOP28. 32k flash. NXP. ARM architecture.

Lab #6
yright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or

5

#### **ARM Cortex Processors**

- For the ARM processors included in your kit a surface mount adapter and soldering is required.
- Adapters, pins, and de-soldering braid (for cleaning after soldering) are included in both the project #1 and #2 kits.

## The PIC32 Microcontroller System

- 1. Hardware: Bare IC in breadboard.
- 2. Development environment: XC32 from Microchip. (Derived from GCC but...)
- 3. Flash Loader: Pro32 via BO230XS board by yours truly.
- 4. Workflow: via Makefiles in CrossIDE or VS code. Examples in Canvas.

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or

7

#### **The PIC32 Microcontroller System** ממע AVDD TXD USB RB8 RB9 RB7 RB7 RB1 LC32SWX130 RXI VCAP RTS 100µF AVSS (27) CBUS3 is pin 6 of J3 in BO230XS board 8 Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.


# The PIC32 Microcontroller System

Qty	Supplier's#	Man's #	Description
2	BC1148CT-ND	K104Z15Y5VE5TL2	CAP CER 0.1UF 25V Y5V RADIAL
2	BC1157CT-ND	K105Z20Y5VE5TH5	CAP CER 1UF 25V Y5V RADIAL
2	330QBK-ND	CFR-25JB-52-330R	RES 330 OHM 1/4W 5% AXIAL
1	67-1102-ND	SSL-LX5093HD	LED RED DIFF 5MM ROUND T/H
1	67-1108-ND	SSL-LX5093LGD	LED GRN DIFF 5MM ROUND T/H
1	MCP1700-3302E/TO-ND	MCP1700-3302E/TO	IC REG LDO 3.3V 0.25A TO92-3
1	PIC32MX130F064B-I/SP-ND	PIC32MX130F064B-I/SP	IC MCU 32BIT 64KB FLASH 28SDIP
1	493-1548-ND	UHE1E101MED	CAP ALUM 100UF 20% 25V RADIAL
2	P8070SCT-ND	EVQ-11A04M	SWITCH TACTILE SPST-NO 0.02A 15V

Lab #6
ht © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used,

9

# The PIC32 Microcontroller System

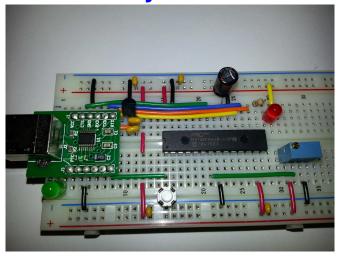


Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## The MSP430 Microcontroller System

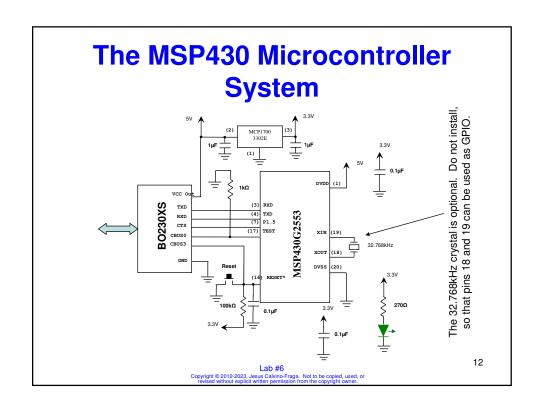- 1. Hardware: Bare IC + Adapter in breadboard.
- Development environment: GCC for MSP430.
- 3. Flash Loader: MSP430\_prog via BO23XS board by yours truly.
- 4. Workflow: via makefiles in CrossIDE or VS code. Examples in Canvas.

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or




# The MSP430 Microcontroller System

Quantity	Digi-Key Part #	Description
3	BC1148CT-ND	0.1uF ceramic capacitors
2	BC1157CT-ND	1uF ceramic capacitor
2	270QBK-ND	270Ω resistor
1	1.0KQBK-ND	1kΩ resistor
1	100KQBK-ND	100kΩ resistor
1	MCP1700-3302E/TO-ND	IC REG LINEAR 3.3V 250MA TO92-3
1	67-1108-ND	LED 5MM GREEN
-1	300-8842-ND	CRYSTAL 32.7680KHZ 7PF T/H
1	296-28429-5-ND	MSP430G2553
1	P8070SCT-ND	Push button switch

Lab #6
copyright @ 2012-2023, Jesus Calvino-Fraga. Not to be copied, used

13

# The MSP430 Microcontroller System

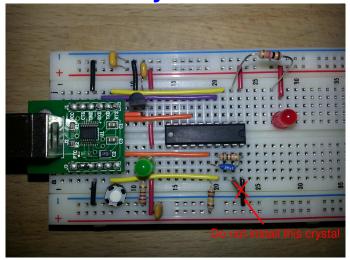

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## The ATMEGA328P Microcontroller System

- 1. Hardware: Bare IC in breadboard.
- 2. Development environment: Atmel AVR 8-bit Toolchain for Windows.
- 3. Flash Loader: spi\_atmega328 via BO230XS board by yours truly.
- 4. Workflow: via Makefiles in CrossIDE or VS code. Examples in Canvas.

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or

15

#### The ATMEGA328P **Microcontroller System** (2) RXD (3) TXD VCC Out AVDD MOSI (17) USB RXD (18) MISO RTS 16.000MHz AVSS RESET\* (8) 330Ω 16


## The ATMEGA328P Microcontroller System

Qty	Supplier's#	Man's #	Description
3	BC1148CT-ND	K104Z15Y5VE5TL2	CAP CER 0.1UF 25V Y5V RADIAL
1	1.0KQBK-ND	CFR-25JB-52-1K	RES 1K OHM 1/4W 5% AXIAL
2	330QBK-ND	CFR-25JB-52-330R	RES 330 OHM 1/4W 5% AXIAL
1	67-1102-ND	SSL-LX5093HD	LED RED DIFF 5MM ROUND T/H
1	67-1108-ND	SSL-LX5093LGD	LED GRN DIFF 5MM ROUND T/H
1	CTX1085-ND	ATS16B	CRYSTAL 16.0000MHZ 18PF T/H
1	ATMEGA328P-PU-ND	ATMEGA328P-PU	IC MCU 8BIT 32KB FLASH 28DIP
1	P8070SCT-ND	EVQ-11A04M	SWITCH TACTILE SPST-NO 0.02A 15V

Lab #6
2012-2023, Jesus Calvino-Fraga. Not to be copied, used, of

17

## The ATMEGA328P Microcontroller System

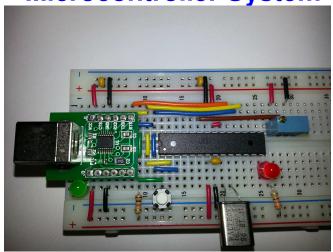


Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## The STM32L051 Microcontroller System

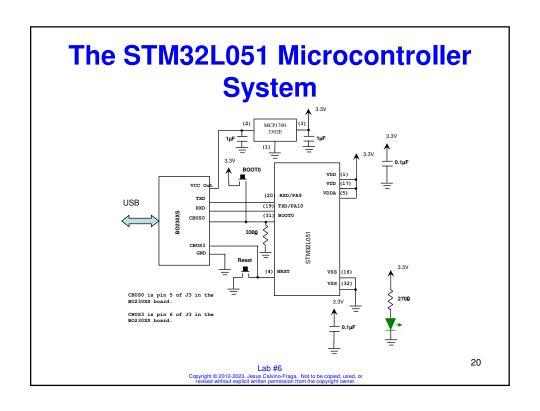- 1. Hardware: Bare IC + Adapter in breadboard.
- 2. Development environment: GCC for ARM.
- 3. Flash Loader: stm32flash.
- 4. Workflow: via Makefiles in CrossIDE. Examples in Connect.

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.




## The STM32L051 Microcontroller System

Quantity	Digi-Key Part #	Description
2	BC1148CT-ND	0.1uF ceramic capacitors
2	BC1157CT-ND	1uF ceramic capacitors
2	270QBK-ND	270Ω resistor
1	330QBK-ND	330Ω resistor
1	67-1102-ND	LED 5MM RED
1	67-1108-ND	LED 5MM GREEN
1	MCP1700-3302E/TO-ND	MCP17003302E 3.3 Voltage Regulator
1	N/A	BO230XS USB adapter
1	497-14901-ND	STM32L051K8T6
1	1528-1065-ND	LQFP32 to DIP32 adapter board
2	A26509-16-ND	16-pin header connector
1	P8070SCT-ND	Push button switch

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, o

21

## The STM32L051 Microcontroller System

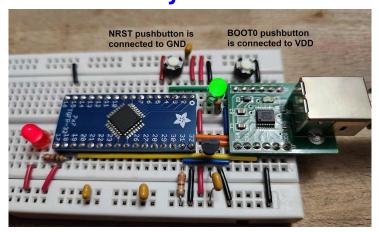


Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

## The LPC824 Microcontroller System

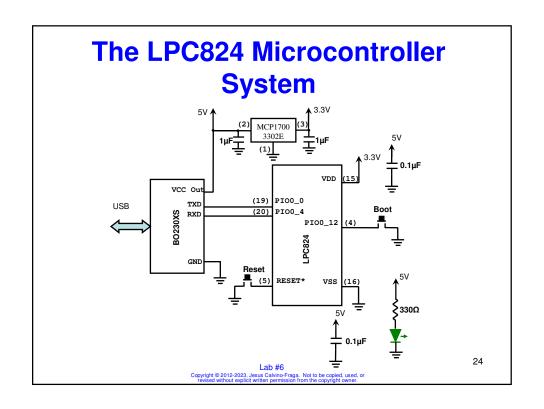- 1. Hardware: Bare IC + Adapter in breadboard.
- 2. Development environment: GCC for ARM.
- 3. Flash Loader: Port of lpc21isp via BO23XS board.
- 4. Workflow: via makefiles in CrossIDE. Examples in Connect.

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or




#### **The LPC824 Microcontroller System**

Qty	Supplier's# Man's #		Description	
2	BC1148CT-ND	K104Z15Y5VE5TL2	CAP CER 0.1UF 25V Y5V RADIAL	
2	BC1157CT-ND	K105Z20Y5VE5TH5	CAP CER 1UF 25V Y5V RADIAL	
1	1.0QBK-ND	CFR-25JB-52-1R	RES 1 OHM 1/4W 5% AXIAL	
1	330QBK-ND	CFR-25JB-52-330R	RES 330 OHM 1/4W 5% AXIAL	
1	67-1102-ND	SSL-LX5093HD	LED RED DIFF 5MM ROUND T/H	
1	67-1108-ND	SSL-LX5093LGD	LED GRN DIFF 5MM ROUND T/H	
1	MCP1700-3302E/TO-ND	MCP1700-3302E/TO	IC REG LDO 3.3V 0.25A TO92-3	
1	568-11619-1-ND	LPC824M201JDH20J	IC MCU 32BIT 32KB FLASH 20TSSOP	
0.33	1528-1066-ND	1206	SMT ADAPTERS 3 PACK 20SOIC/TSSOP	
2	A26509-10-ND	4-103741-0-10	CONN HEADR BRKWAY .100 10POS STR	
2	P8070SCT-ND	EVQ-11A04M	SWITCH TACTILE SPST-NO 0.02A 15V	

Total

25
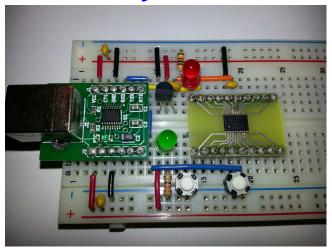
#### **The LPC824 Microcontroller System**



Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

#### Which one to Pick?

- Size of the documentation:
  - ATMega328P: 294 pages
  - MSP430: 644+76 pages
  - PIC32: 1138+344 pages
  - LPC824: 487+82 pages
  - STM32L051: 784+133 pages
- Quality of the documentation (personal opinion):
  - ATMega328P: ok
  - MSP430: ok
  - PIC32: Excellent
  - LPC824: Excellent
  - STM32L051: Very good.

I ah #6

Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used revised without explicit written permission from the copyright owner.

27

#### Which one to Pick?

- Raw power:
  - ATMega328P: ok
  - MSP430: Good
  - PIC32: Excellent
  - STM32L051: Excellent
  - LPC824: 60MHz! The fastest of the bunch.
- Examples:
  - ATMega328P: Excellent. Everywhere!
  - MSP430: Good
  - PIC32: Good (in the manual!)
  - STM32L051: Good (in the manual!)
  - LPC824: Good (in the manual!)
- Number of timers (I may be wrong):
  - ATMega328P: 1 x 16-bits, 2 x 8-bits.
  - MSP430: 2 x 16-bit (each with two channels)
  - PIC32: 5 x 16-bit
  - STM32L051: 4 x 16 bit, 1 x 24 bit. TIM2 has four channels. TIM21 and TIM22 have two channels. TIM6 has one channel. SysTick.
  - LPC824: 4 x 16 bit + SCTimer + SysTick.


28

Lab #6
Copyright © 2012-2023. Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.
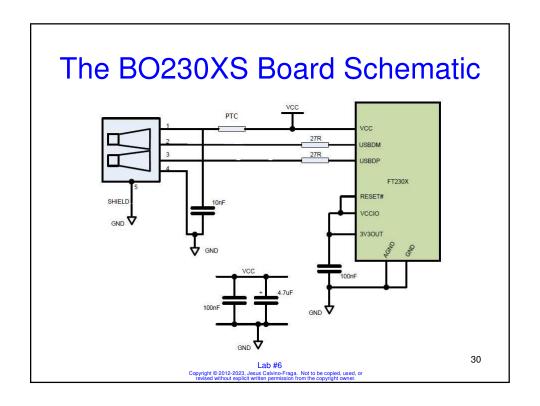
#### The BO230XS Board

- The BO230XS is a minimal system around the FT230XS IC that allows for communication between a Computer (using USB) and a microcontroller system.
- It can be used as serial port interface or a SPI interface using libraries and drivers provided by the manufacturer.
- Permits the implementation of simple flash memory programmers via boot loaders and SPI.

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or



#### The FT230XS Board

Qty	Supplier's#	Man's #	Description
1	768-1135-1-ND	FT230XS-R	IC USB SERIAL BASIC UART 16SSOP
2	A26509-06-ND	4-103741-0-06	CONN HEADR BRKWAY .100 06POS STR
1	ED2983-ND	USB-B1HSB6	CONN USB TYPE B R/A BLACK
2	399-1170-1-ND	C0805C104K5RACTU	CAP CER 0.1UF 50V X7R 0805
2	P27ACT-ND	ERJ-6GEYJ270V	RES SMD 27 OHM 5% 1/8W 0805
1	478-8222-1-ND	F931A475MAA	CAP TANT 4.7UF 10V 20% 1206
1	507-1797-1-ND	0ZCJ0020FF2E	PTC RESTTBLE 0.20A 30V CHIP 1206
1			PCB from PCBCart

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

31

#### **BO230XS** replacement

- Boards that use either the FT230XS or FT231XS ICs are ok.
- Inexpensive option from DigiKey (\$14.27):
  - LC231X.
  - Digi-Key Part Number: 768-1316-ND.
  - You'll need to solder the header pins.

32

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, revised without explicit written permission from the copyright owner.


#### Examples Relevant to Lab #6


- ATMega328:
  - LCD and Period.
- MSP430:
  - LCD and Period.
- PIC32MX130:
  - LCD and Period.
- STM32L051:
  - LCD and Period.
- LPC824:
  - LCD and Period.

Lab #6
ight © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or


33
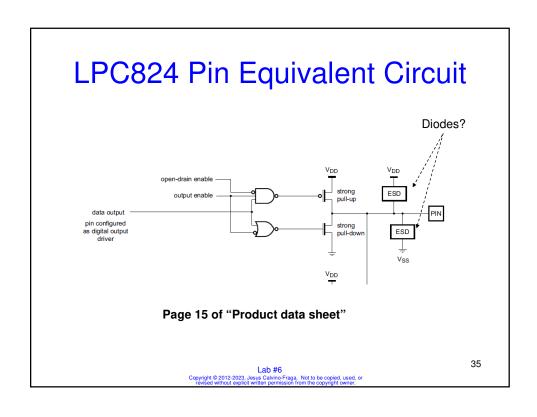
# ATMega328P Pin Equivalent Circuit Figure 14-1. I/O Pin Equivalent Schematic See Figure "General Digital I/O" for Details Lab #6 Copyright = 2910-2023. Jestifical Pigens Report to be acquired, mean of a second contact of the second contact of the second without despital contact of the second contact of



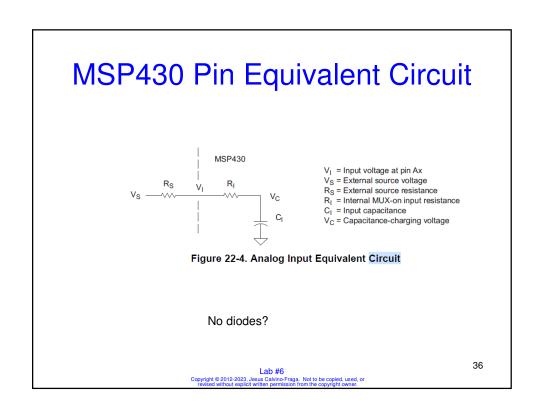

#### PIC32MX130 Pin Equivalent Circuit

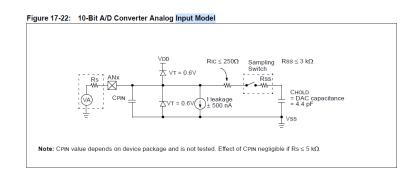

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used,


37

#### STM32L051 Pin Equivalent Circuit

Electrical characteristics

STM32L051x6 STM32L051x8


Figure 29. Typical connection diagram using the ADC

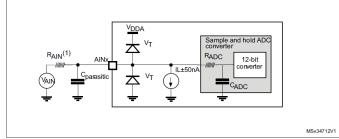

38

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

#### Recommended Circuit for Lab #6

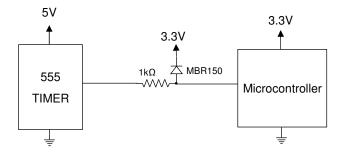

Since the ATMega328P power is 5V, no protection circuit is needed.

The diode is only needed if using the MSP430G2553.

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used,

39

#### macOS support

- As of the moment of writing this, the only processors supported in macOS are the LPC824 and STM32L051. Instructions posted on Canvas.
- The LPC824 and the STM32L051 are the only ones that come with a proper serial boot loader from factory.
- (The MSP430 has also a serial boot loader, but the programming pins are a mess! Therefore it doesn't work on macOS.)

40

Lab #6
Copyright © 2012-2023, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.